

Embedded systems 2

# Report Cosy Cafeteria

Robin Van de Poel      Arthur Van den Storme  
Tobias Cromheecke      Thomas Feys

April 3, 2020

# Contents

<b>1</b>	<b>Intro</b>	<b>3</b>
<b>2</b>	<b>Functionality</b>	<b>3</b>
<b>3</b>	<b>Hardware design</b>	<b>3</b>
3.1	Power management . . . . .	3
3.1.1	Battery charging circuit . . . . .	3
3.1.2	Battery protection circuit . . . . .	3
3.1.3	Polarity protection . . . . .	3
3.2	Microcontroller . . . . .	3
3.3	Sensorboard . . . . .	3
<b>4</b>	<b>Dimensioning components</b>	<b>3</b>
4.1	Charging . . . . .	3
4.1.1	Charge Current Translator . . . . .	4
4.2	System enable input . . . . .	4
4.3	Calculations . . . . .	5
4.3.1	Program the Fast Charge Current $I_{CHG}$ . . . . .	5
4.3.2	Program the Input Current Limit $I_{LIM}$ . . . . .	5
4.3.3	Fast-Charge Safety Timer (TMR) . . . . .	5
4.3.4	TS function . . . . .	6
4.3.5	Selecting IN, OUT, and BAT Pin Capacitors . . . . .	6
4.3.6	Selecting MOSFETs . . . . .	6
<b>5</b>	<b>Energy management - autonomy</b>	<b>6</b>
<b>6</b>	<b>Wireless connectivity</b>	<b>6</b>
<b>7</b>	<b>Financial estimate</b>	<b>6</b>
<b>8</b>	<b>Validation and measurements</b>	<b>6</b>

## 1 Intro

- url's github - wat gaat uw systeem juist doen

## 2 Functionality

ofwel in intro vermelden?

## 3 Hardware design

### 3.1 Power management

#### 3.1.1 Battery charging circuit

#### 3.1.2 Battery protection circuit

#### 3.1.3 Polarity protection

### 3.2 Microcontroller

### 3.3 Sensorboard

## 4 Selection battery

## 5 Selection battery charger components

There are many manufacturers who produce charging IC's bla bla bla ...

We considered many chips from different kind of manufacturers. Eventually we went with the BQ24075 IC from Texas Instruments. It's a great chose because it's made to charge a single cell Li-Ion battery (that's all we need), and it's perfectly fit to charge using a USB port because the IC has a selectable 100 mA and 500 mA maximum input current **TO DO: VERWIJZEN NAAR USB TABEL. OOK NOG ZEGGEN DAT DE OPLAADSTROOM OVEREENKOMT MET DIE VAN DE BATTERY.** In the subsections below you'll find the calculations.

### 5.1 Charging

Set  $\overline{CE}$  low to initiate battery charging. The battery is charged in three phases:

1. Conditioning pre-charge
2. Constant current fast charge (current regulation)
3. Constant voltage tapering (voltage regulation)

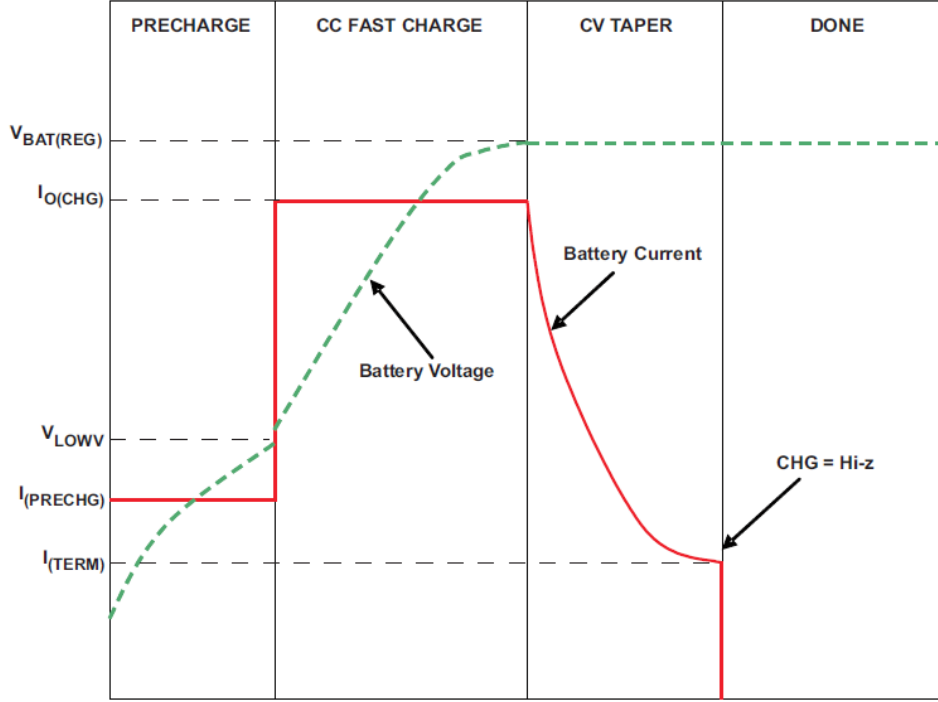


Figure 1: Charge cycle

In the pre-charge phase, the battery is charged at with the pre-charge current  $I_{PRECHG}$ . Once the battery voltage crosses the  $V_{LOWV}$  threshold, the battery is charged with the fast-charge current  $I_{CHG}$ . As the battery voltage reaches  $V_{BAT(REG)}$ , the battery is held at a constant voltage of  $V_{BAT(REG)}$  and the charge current tapers off as the battery approaches full charge. When the battery current reaches  $I_{TERM}$ , the CHG pin indicates charging done by going high-impedance.

The value of the fast-charge current is set by the resistor connected from the ISET pin to VSS, and is given by the equation:

$$I_{CHG} = \frac{K_{ISET}}{R_{ISET}}$$

The charge current limit is adjustable up to 1.5 A. The valid resistor range is 590  $\Omega$  to 8.9 k $\Omega$ . If  $I_{CHG}$  is programmed as greater than the input current limit, the battery will not charge at the rate of  $I_{CHG}$ , but at the slower rate of  $I_{IN(MAX)}$  (minus the load current on the OUT pin, if any). In this case, the charger timers will be proportionately slowed down.

### 5.1.1 Charge Current Translator

When the charger is enabled, internal circuits generate a current proportional to the charge current at the ISET input. The current out of  $I_{SET}$  is 1/400 ( $\pm 10\%$ ) of the charge current. This current, when applied to the external charge current programming resistor,  $R_{ISET}$ , generates an analog voltage that can be monitored by an external host to calculate the current sourced from BAT.

$$V_{ISET} = \frac{I_{CHG}}{400} R_{ISET}$$

## 5.2 System enable input

Connect SYSOFF high to turn off the FET connecting the battery to the system output. When an adapter is connected, charging is also disabled. Connect SYSOFF low for normal operation. SYSOFF is internally pulled up to VBAT through a large resistor (approximately 5 M $\Omega$ ). Do not leave SYSOFF unconnected to ensure proper operation.

## 5.3 Calculations

### 5.3.1 Program the Fast Charge Current $I_{CHG}$

$$R_{ISET} = \frac{K_{ISET}}{I_{CHG}}$$

From the electrical table we can find:

$$K_{ISET} = 890A\Omega$$

The charge current limit is adjustable up to 1.5 A. The maximum charge current for the Panasonic NCR18650B battery is 1625 mA. Set the charge current to 1.3 A to have some margin for the battery lifetime.

$$R_{ILIM} = \frac{890A\Omega}{1.3A} = 684.62\Omega \approx 680\Omega$$

The valid resistor range is 590  $\Omega$  to 8.9 k $\Omega$ . Select the closest standard value, which for this case is 680  $\Omega$ . Connect this resistor between ISET (pin 16) and VSS.

$$I_{CHG} = \frac{890A\Omega}{680\Omega} = 1.31A$$

### 5.3.2 Program the Input Current Limit $I_{LIM}$

$$R_{ILIM} = \frac{K_{ILIM}}{I_{IN(MAX)}}$$

From the electrical table we can find:

$$K_{ILIM} = 1610A\Omega$$

The input current limit is adjustable up to 1.5 A. Set the input current limit higher than the charge current of 1.3 A.

$$R_{ILIM} = \frac{1610A\Omega}{1.5A} = 1.073k\Omega \approx 1.1k\Omega$$

The valid resistor range is 1.1 k $\Omega$  to 8 k $\Omega$ . Select the closest standard value, which for this case is 1.1 k $\Omega$ . Connect this resistor between ILIM (pin 12) and VSS.

$$I_{ILIM} = \frac{1610A\Omega}{1.1k\Omega} = 1.46A$$

### 5.3.3 Fast-Charge Safety Timer (TMR)

Leave TMR open to set to default safety timers. Connect to VSS to disable safety timers.

### 5.3.4 TS function

Connect a 10 k $\Omega$  resistor from TS to VSS to set the TS voltage at a valid level and maintain charging.

### 5.3.5 Selecting IN, OUT, and BAT Pin Capacitors

In most applications, all that is needed is a high-frequency decoupling capacitor (ceramic) on the power pin, input, output and battery pins. Using the values shown on the application diagram, is recommended. After evaluation of these voltage signals with real system operational conditions, one can determine if capacitance values can be adjusted toward the minimum recommended values (DC load application) or higher values for fast high amplitude pulsed load applications. Note if designed high input voltage sources (bad adaptors or wrong adaptors), the capacitor needs to be rated appropriately. Ceramic capacitors are tested to 2x their rated values so a 16-V capacitor may be adequate for a 30-V transient (verify tested rating with capacitor manufacturer).

### 5.3.6 Selecting MOSFETs

Discharge Overcurrent Detection (OCD) voltage = 100 mV.  $R_{DS(ON)} = 30m\Omega @ V_{GS} = 4.5V$  Maximum operating discharge current =  $\frac{100mV}{2*30m\Omega} = 1.67A$

## 6 Energy management - autonomy

Berekeningen voor levensduur komen hier.

## **7 Wireless connectivity**

@Thomas ik zou voorstellen hier de wifi dingen te vermelden?

## **8 Financial estimate**

Kostprijs van het project opstellen.

## **9 Validation and measurements**

Hier moeten we aantonen of dat alles werkt. Of eventuele fouten verklaren.